

二进制状态转移表:

X \ Q ₁ Q ₀	00	01	11	10
0	00/0	00/0	00/0	X
1	01/0	11/0	11/1	X

状态方程:

$\Rightarrow D_0 = X$

X \ Q ₁ Q ₀	00	01	11	10
0	0	0	0	X
1	1	1	1	X

$D_1 = X Q_0$


X \ Q ₁ Q ₀	00	01	11	10
0	0	0	0	X
1	0	1	1	X

输出方程:

$Y = X Q_1$

X \ Q ₁ Q ₀	00	01	11	10
0	0	0	0	X
1	0	0	1	X
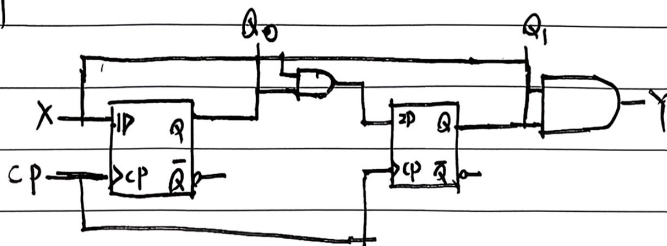
$$\begin{cases} D_0 = X \\ D_1 = X Q_0 \\ Y = X Q_1 \end{cases} \Rightarrow$$



能够自启动

key step: 状态转移图 \Rightarrow 状态转移真值表 \Rightarrow 所有输入组合的状态, 输出
 \Rightarrow 根据卡诺图写激励方程 (选择合适的角线)
 \Rightarrow 根据激励方程画逻辑图

