

Verilog 代码设计.

// Moore - 101 检测

```
module Moore101 (
```

```
    input wire clk,
```

```
    input wire rst_n,
```

```
    input wire cin,
```

```
    output reg detected
```

```
);
```

```
parameter S0 = 2'b00;
```

```
parameter S1 = 2'b01;
```

```
parameter S2 = 2'b10;
```

```
parameter S3 = 2'b11;
```

```
reg [1:0] cur_st, next_st;  
always @ (posedge clk or  
         negedge rst_n) begin  
    if (!rst_n) cur_st <= S0;  
    else cur_st <= next_st;  
end // 状态寄存器
```

```
always @ (*) begin  
    case (cur_st)  
        S0: next_st = (cin == 1'b1)?  
            S1: S0;  
        S1: next_st = (cin == 1'b0)?  
            S2: S1;  
        S2: next_st = (cin == 1'b1)?  
            S3: S0;  
    endcase
```

```
s3: next_st = (cin == 1'b1) ?  
    s1: s2;  
    default: next_st = s0;  
endcase  
end
```

```
always @ (*) begin  
    detected = (cur_st == s3) ?  
        1'b1 : 1'b0;  
end // 摩尔型输出只和状态有关.
```

```
endmodule.
```

//. Mealy_101检测.

```
module Mealy101(  
    input wire clk,  
    input wire rst_n,  
    input wire cin,  
    output reg detected  
);
```

```
    parameter S0 = 2'b00;
```

```
    parameter S1 = 2'b01;
```

```
    parameter S2 = 2'b10;
```

```
    reg [1:0] cur_st, next_st;
```

```
    always @(posedge clk or  
            negedge rst_n) begin
```

```
if (!rst_n) cur_st <= S0;  
else cur_st <= next_st;  
end.  
end
```

```
always @(*) begin // @ (cin or cur_st)  
    case (cur_st)
```

```
        S0: begin
```

```
            next_st = cin ? S1 : S0;
```

```
            detected = 1'b0;
```

```
        end
```

```
        S1: begin.
```

```
            next_st = (!cin) S2 : S1;
```

```
            detected = 1'b0;
```

```
        end
```

```
S2: begin
```

```
    next_st = cin ? S1 : S0;
```

```
    detected = cin ? 1'b1 : 1'b0;
```

```
end.
```

```
default: begin.
```

```
    next_st = S0;
```

```
    detected = 1'b0;
```


```
end
```

```
endcase
```

```
end
```

```
endmodule
```

11.2K: Q 触发器检测 101 序列.

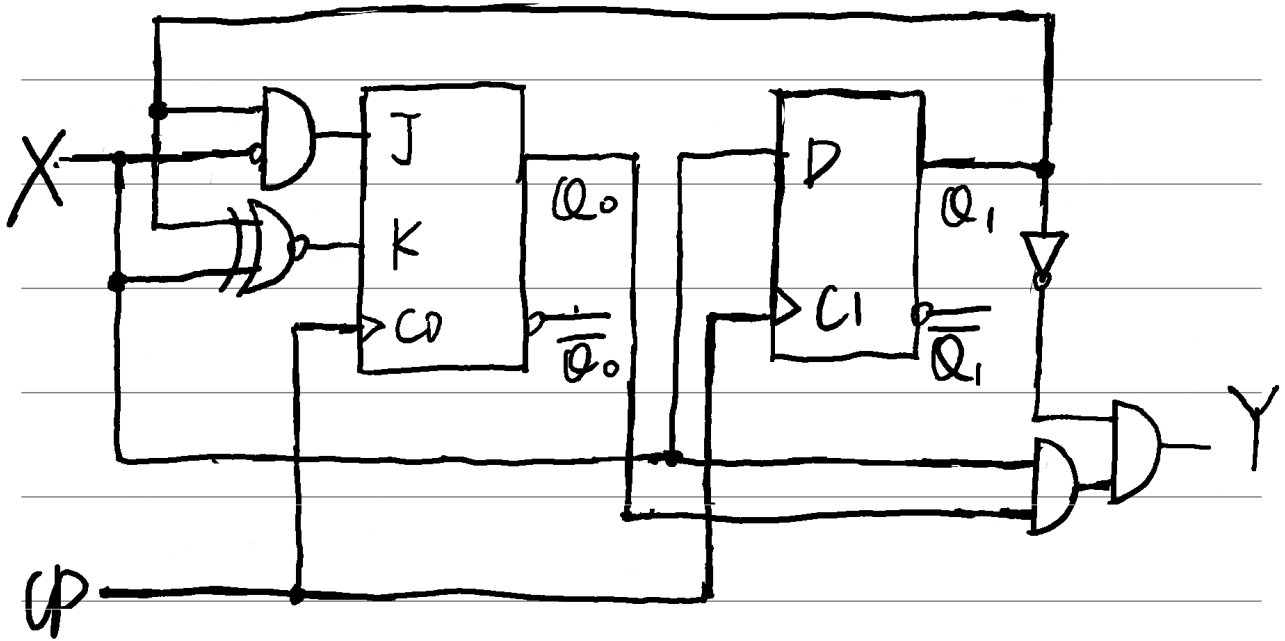

```

module JK101(
    input wire clk,
    input wire rst-n,
    input wire cin,
    output wire detected
);

```

```
wire Q0, Q1; // 输入
```

```
wire J0, K0, D1; // 输出.
```

```
JK_FF JKD (.clk(clk), .rst_n(rst_n),  
            .J(J0), .K(K0), .Q(Q0));
```

```
D_FF D1 (.clk(clk), .rst_n(rst_n),  
          .D(D1), .Q(Q1));
```

```
assign J0 = ~cin & Q1;
```

```
assign K0 = cin ^ Q1;
```

```
assign D1 = cin;
```

```
assign detected = Q0 & ~Q1 & cin;
```

```
endmodule
```


// 4位计数器.

module counter (

input wire load, // 加载指定数据

input wire en, // 使能时计数.

input wire clk,

input wire rst_n,

output reg q,

input wire [3:0] cin,

output reg [3:0] cout

);

always @ (posedge clk or

negedge rst_n) begin

if (!rst_n) begin

cout <= 4'b0000;

```
q <= 1'b0;
end else if (load) begin
    cout <= cin
end else if (en) begin
    if (cout == 4'b1111) begin
        cout <= 4'b0000;
        q <= 1'b1;
    end else begin
        cout <= cout + 1;
    end
end.
end.
end.
endmodule
```

// 异步清零 D 触发器.

```
module DFF (
```

```
    input wire clk,
```

```
    input wire rst_n,
```

```
    input wire D,
```

```
    output reg Q
```

```
);
```

```
    always @ (posedge clk or  
               negedge rst_n) begin
```

```
        if (!rst_n) Q <= 1'b0;
```

```
        else Q <= D;
```

```
    end
```

```
endmodule. // 异步复位, 同步时钟.
```

// 同步 D 触发器.

```
module DFF (
```

```
    input wire clk,
```

```
    input wire rst_n,
```

```
    input wire D,
```

```
    output reg Q
```

```
);
```

```
    always @(posedge clk) begin.
```

```
        if (!rst_n) Q <= 1'b0;
```

```
        else Q <= D;
```

```
    end.
```

```
endmodule.
```

// 要等待时钟才能复位.

// 异步D触发器 (无时钟)

```
module DFF (
```

```
    input wire en,
```

```
    input wire D,
```

```
    output reg Q
```

```
);
```

```
    always @ (en or d) begin
```

```
        if (en) Q = D;    // 无效时锁存
```

```
    end.
```

```
endmodule.
```

// 同步清零的移位寄存器.

```
module shift_register (
```

```
    input wire clk,
```

```
    input wire rst,
```

```
    input wire cin,
```

```
    output wire cout
```

```
);
```

```
    reg [7:0] shift_reg; // 8位寄存器
```

```
    always @(posedge clk)
```

```
        if (rst) begin
```

```
            shift_reg <= 8b'00000000;
```

```
        end else begin
```

```
            shift_reg <= {shift_reg[6:0], cin};
```

```
        end
```

end

assign cout = shift_reg[7];

endmodule

// D 锁存器:

```
module D_latch (
```

```
    input wire clk,
```

```
    input wire D,
```

```
    output wire Q
```

```
);
```

```
    always @(*) begin
```

```
        if (clk) Q = D; // 电平敏感
```

```
    end
```

```
/* always @(posedge clk) begin
```

```
    Q <= D; // 边沿敏感.
```

```
end. // 触发器.
```

```
*/
```

```
endmodule
```


// 16个8位数据的存储器

```
module memory (
```

```
    input wire clk,
```

```
    input wire we, //写使能
```

```
    input wire [3:0] addr,
```

```
    input wire [7:0] cin,
```

```
    output wire [7:0] cout
```

```
);
```

```
    reg [7:0] mem [0:15];
```

// 16个8位存储单元, [0:15]地址范围
深度

```
    always @ (posedge clk) begin
```

```
        if (we) mem [addr] <= cin;
```

```
    end.
```

```
always @ (*) begin  
    cout = mem[addr];  
end.
```

```
/* 写操作 (同步) \  
\ 读操作 (异步) */
```

```
/* 同步读写 \
```

```
always @ (posedge clk) begin  
    if (we) mem[addr] <= cin;  
    cout <= mem[addr];  
end
```

```
\ */  
endmodule
```

// n位移位寄存器

```
module shift_n #(
    parameter n = 16
)(
```

```
    input wire [n-1:0] R,
```

```
    output reg [n-1:0] Q,
```

```
    input wire L,
```

```
    input wire W,
```

```
    input wire clk
```

```
);
```

```
always @(posedge clk) begin.
```

```
    if (L) Q <= R;
```

```
    else begin
```

```
        Q[n-2:0] <= Q[n-1:1];
```

$Q[n-1] \leq w$; //右移.

end.

end.

endmodule.

/* $Q \leq \{w, Q[n-1=1];\}$. \

\ 拼接更直观 */

// 4选1多路选择器

```
module mux4 (
```

```
    input wire d0,
```

```
    input wire d1,
```

```
    input wire d2,
```

```
    input wire d3,
```

```
    input wire [1:0] sel,
```

```
    output reg out.
```

```
);
```

```
always @(sel) begin.
```

```
    case (sel)
```

```
        2'b00: out = d0;
```

```
        2'b01: out = d1;
```


```
        2'b10: out = d2;
```

```
        2'b11: out = d3;
```

endcase

end

endmodule

 

// 异步复位 串联T触发器.

```
module tff2 (
```

```
    input wire data, clk, rst,
```

```
    output reg q
```

```
);
```

```
    reg q1 ;
```

```
    always @(posedge clk or negedge  
            rst) begin.
```

```
        if (!rst) begin
```

```
            q1 <= 0;
```

```
            q <= 0;
```

```
        end else begin.
```



```
            q1 <= q1 ^ data;
```

```
            q <= q ^ q1;
```

end.

end.

endmodule.

  

// 奇偶校验.

```
module check_parity (  
    input wire [31:0] data,  
    output wire even,  
    output wire odd  
);
```

```
    reg check; integer i;  
    always @ (*) begin.
```

```
        check = 1'b0;
```

```
        for (i = 0; i < 32; i = i + 1) begin  
            check = check ^ data[i];
```

```
        end.
```

```
    end.
```

```
    assign even = check, odd = ~check;  
endmodule
```

/* 归约操作符

assign even = ^ data

assign odd = ~ ^ data.

*/

// 4位数值比较.

```
module cmp (
```

```
    input wire [3:0] A,
```

```
    input wire [3:0] B,
```

```
    output wire A_bigger,
```

```
    output wire B_bigger,
```

```
    output wire equal
```

```
);
```

```
    assign A_bigger = (A > B);
```

```
    assign B_bigger = (B > A);
```

```
    assign equal = (A == B);
```

```
endmodule
```